

## Lab 5: Seven Segment Display

### 1) Purpose

Aim of this lab is to understand how to use 7 segment display on the Basys 3 FPGA board and design a digital circuit using 7 segment display. A design that can be show 4 different digits simultaneously should be made. In this lab a design that can take 16 values from 4 different switches for each 4 digits is used. The 4 digit display shows each digit simultaneously according to given 16 switch inputs (4 switch for each 4 digit).

### 2) Questions

1) What is the internal clock frequency of Basys 3?

a) A 100Mhz internal clock is included in Basys 3.

2) How can you create a slower clock signal from this one?

a) To create a slower clock frequency we can create another signal and assign its value to '1' and '0' according to a timer derived from the internal clock. For example, we can assign a number and increase it at the time when each rising edge of internal clock appears up to a constant value n. Then when the number reaches n the signal we define changes the value such as from '1' to '0' or vice versa. An example function is given below.

```
process(clk)
begin
  if(rising_edge(clk)) then
    divider <= divider + 1;
  end if;
  if (divider = n) then
    timer <= not(timer);
    Divider = 0;
  end if;
end process;
```

Figure 2.1 Example lower frequency clock

3) Can you create a clock with any arbitrary frequency lower than that of the internal clock?

a) We can create lower frequencies using the method mentioned above.

But its value will be  $100\text{MHz}/n$  since in each cycle 1 rising edge appears in internal clock but we assign our signal to change value when  $n$  cycle appears. Therefore, we can get lower frequency signals with frequency  $100\text{MHz}/n$  for  $n$  being positive integer.

### 3) Methodology

As the 4 digit's cathodes are in parallel it is impossible to display 4 different digits simultaneously. However, as human eye can detect 30-60 frames per second (30fps videos are 30 photos shown in 1 second and we interpret it as a continuous frame) and an optic effect called persistence of vision explained as as soon as photons stop encountering the eye, optic nerves do not respond simultaneously after a short period of time the perception of light disappears, we show each digit at a time with a frequency ( $100\text{MHz}/2^{18} = 381.5\text{Hz}$ ) higher than human eye detect. But we arrange the frequency so that the led of the 7 segment display is not damaged (frequency lower than  $1\text{kHz}$ ).

We assigned a 20 bit signal and incremented it by 1 with each rising edge appearing in internal clock of Basys 3 using IEEE.STD\_LOGIC\_UNSIGNED library. Then we used its most significant 2 digits as our digit selection signal with frequency ( $100\text{MHz}/2^{18} = 381.5\text{Hz}$ ). We used a decoder to choose which anode will be 0 and others 1 (o anode means digit is active and lighted on regarding to cathode signal). According to 2 bit signal we derived we choose digits and by using another multiplexer with the same selection signal we assign cathode signal derived from given 4 bit input for that digit by user revealing the

pattern of the digit. For each 4 digit and 16 characters determined by user given input assigned and sent to 7 segment display and shown with the frequency mentioned above. Schematic of the circuit can be seen in the figure below.

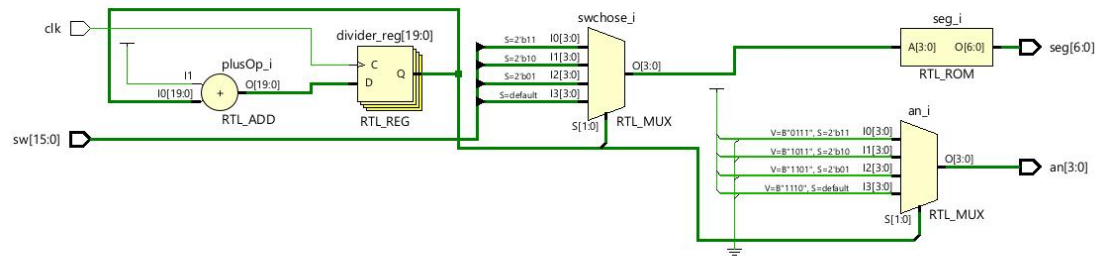


Figure 3.1 schematic of the design. sw user determined 4x4 input, clk internal clock of Basys 3, seg cathode output signal of 7 segment display, an anode output signal of 7 segment display

And the VHDL design code constraint file and test bench codes written in the appendix .

#### 4) Results

Test bench simulation result and results gotten from implementation in Basys 3 can be seen the figures below. As in test bench mode signals assigned regarding to a given time period in order for the given 4 simulation value to be assigned its running time set to 1ms.



 


Figure 4.3 sw (0100 0011 0010 0001) showing 4321 as expected

 


Figure 4.4 sw (1010 1111 1100 1101) showing afcd as expected (hexadecimal digits)



 


Figure 4.5 sw (1010 1011 1100 1101) showing abcd as expected (hexadecimal digits)

 


Figure 4.6 sw (0001 1000 1000 0001) showing 1881 as expected

 


Figure 4.7 sw (0001 1001 0010 0011) showing 1923 as expected

## 5) Conclusion

In conclusion we learned internal structure of the 7 segment display (reference annual of the Basys 3 board includes detailed explanations for the cathode parallelity anode configuration and the cathode signals that should be sent to display different configurations in each digit) and we learned how to divide internal clock signal of Basys 3 and used it for displaying 4 different digits simultaneously by using optic persistence phenomena of human eye.

## 6) Appendix

- Design code

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

entity deneme is

```
    Port ( sw : in std_logic_vector (15 downto 0);
```

```
          clk : in std_logic;
```

```
          seg : out std_logic_vector (6 downto 0);
```

```
          an : out std_logic_vector (3 downto 0));
```

```
end deneme;
```

architecture Behavioral of deneme is

```
    signal divider: std_logic_vector (19 downto 0):="00000000000000000000";
```

```
    signal swchase: std_logic_vector (3 downto 0):="0000";
```

```
begin
```

```
    process(clk)
```

```
    begin
```

```
        if(rising_edge(clk)) then
```

```
            divider <= divider + 1;
```

```
        end if;
```

```
    end process;
```



with swchose select

```
seg <= "0000001" when "0000", --0
    "1001111" when "0001", --1
    "0010010" when "0010", --2
    "0000110" when "0011", --3
    "1001100" when "0100", --4
    "0100100" when "0101", --5
    "0100000" when "0110", --6
    "0001101" when "0111", --7
    "0000000" when "1000", --8
    "0000100" when "1001", --9
    "0000010" when "1010", --A
    "1100000" when "1011", --B
    "0110001" when "1100", --C
    "1000010" when "1101", --D
    "0110000" when "1110", --E
    "0111000" when "1111", --F
    "1111111" when others; --default
```

with divider(19 downto 18) select

```
swchose <= sw(15 downto 12) when "11",
    sw(11 downto 8) when "10",
    sw(7 downto 4) when "01",
    sw(3 downto 0) when others;
```

```

process(divider(19 downto 18))
begin
  case divider(19 downto 18) is
    when "11" => an <= "0111";
    when "10" => an <= "1011";
    when "01" => an <= "1101";
    when others => an <= "1110";
  end case;
end process;

end Behavioral;

```

- Test bench code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity test is
  -- Port ( );
end test;

architecture Behavioral of test is
  component deneme is
    Port ( sw : in std_logic_vector (15 downto 0);
          clk : in std_logic;
          seg : out std_logic_vector (6 downto 0);

```

```
        an : out std_logic_vector (3 downto 0));  
end component deneme;
```

```
signal an : std_logic_vector(3 downto 0);  
signal seg : std_logic_vector(6 downto 0);  
signal sw : std_logic_vector(15 downto 0);  
signal clk: std_logic := '0';  
constant period : time := 0.1ns;
```

```
begin  
  
UUT: deneme port map(  
  
    an => an,  
  
    seg => seg,  
  
    sw => sw,  
  
    clk => clk  
);
```

```
clock : process
```

```
begin
```

```
wait for period /2;
```

```
clk <= '1';
```

```
wait for period/2;
```

```
clk <= '0';
```

```
end process;
```

```
test : Process
```

```
begin
```

```
sw <= "00000000000110000";
```

```
wait for 0.25 ms;
```

```
sw <= "0011000001110010";
```

```
wait for 0.25 ms;
```

```
sw <= "0010001000010000";
```

```
wait for 0.25 ms;
```

```
sw <= "1010101111001101";
```

```
wait for 0.25 ms ;
```

```
end process;
```

- Constraint file

```
set_property PACKAGE_PIN V17 [get_ports {sw[0]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {sw[0]}]
```

```
set_property PACKAGE_PIN V16 [get_ports {sw[1]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {sw[1]}]
```

```
set_property PACKAGE_PIN W16 [get_ports {sw[2]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {sw[2]}]
```

```
set_property PACKAGE_PIN W17 [get_ports {sw[3]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {sw[3]}]
```

```
set_property PACKAGE_PIN W15 [get_ports {sw[4]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {sw[4]}]
```

```
set_property PACKAGE_PIN V15 [get_ports {sw[5]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {sw[5]}]
```

```
set_property PACKAGE_PIN W14 [get_ports {sw[6]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {sw[6]}]
```

```
set_property PACKAGE_PIN W13 [get_ports {sw[7]}]
```



set\_property IOSTANDARD LVCMOS33 [get\_ports {sw[7]}]  
set\_property PACKAGE\_PIN V2 [get\_ports {sw[8]}]  
set\_property IOSTANDARD LVCMOS33 [get\_ports {sw[8]}]  
set\_property PACKAGE\_PIN T3 [get\_ports {sw[9]}]  
set\_property IOSTANDARD LVCMOS33 [get\_ports {sw[9]}]  
set\_property PACKAGE\_PIN T2 [get\_ports {sw[10]}]  
set\_property IOSTANDARD LVCMOS33 [get\_ports {sw[10]}]  
set\_property PACKAGE\_PIN R3 [get\_ports {sw[11]}]  
set\_property IOSTANDARD LVCMOS33 [get\_ports {sw[11]}]  
set\_property PACKAGE\_PIN W2 [get\_ports {sw[12]}]  
set\_property IOSTANDARD LVCMOS33 [get\_ports {sw[12]}]  
set\_property PACKAGE\_PIN U1 [get\_ports {sw[13]}]  
set\_property IOSTANDARD LVCMOS33 [get\_ports {sw[13]}]  
set\_property PACKAGE\_PIN T1 [get\_ports {sw[14]}]  
set\_property IOSTANDARD LVCMOS33 [get\_ports {sw[14]}]  
set\_property PACKAGE\_PIN R2 [get\_ports {sw[15]}]  
set\_property IOSTANDARD LVCMOS33 [get\_ports {sw[15]}]

set\_property PACKAGE\_PIN W7 [get\_ports {seg[6]}]  
set\_property IOSTANDARD LVCMOS33 [get\_ports {seg[6]}]  
set\_property PACKAGE\_PIN W6 [get\_ports {seg[5]}]  
set\_property IOSTANDARD LVCMOS33 [get\_ports {seg[5]}]  
set\_property PACKAGE\_PIN U8 [get\_ports {seg[4]}]  
set\_property IOSTANDARD LVCMOS33 [get\_ports {seg[4]}]

```
set_property PACKAGE_PIN V8 [get_ports {seg[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[3]}]
set_property PACKAGE_PIN U5 [get_ports {seg[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[2]}]
set_property PACKAGE_PIN V5 [get_ports {seg[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[1]}]
set_property PACKAGE_PIN U7 [get_ports {seg[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[0]}]

set_property PACKAGE_PIN U2 [get_ports {an[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[0]}]
set_property PACKAGE_PIN U4 [get_ports {an[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[1]}]
set_property PACKAGE_PIN V4 [get_ports {an[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[2]}]
set_property PACKAGE_PIN W4 [get_ports {an[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[3]}]

set_property PACKAGE_PIN W5 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports clk]
```